





$$\begin{vmatrix} \frac{d(U_{C1})}{dt} = \frac{i_{L2} + \frac{U_1}{R_3} - U_{C1} \times \left(\frac{1}{R_1} + \frac{1}{R_3}\right)}{C_1} \\ \frac{d(U_{C2})}{dt} = \frac{i_{L2}}{C_2} \\ \frac{d(i_{L2})}{dt} = \frac{U_1 - U_{C1} - U_{C2} - i_{L2} \times (R_2 + R_4)}{L_2} \end{vmatrix}$$

$$U_2 = i_L \times R_4$$

$$value[0]=U_{C1}$$
 $value[1]=U_{C2}$ 
 $value[2]=i_{L2}$